



SEMICONDUCTOR DIODE

Q Why semiconductor?

It enhances the performance, reliability and cost effectiveness of electronic system (information & energy system)

Properties of Semiconductor -


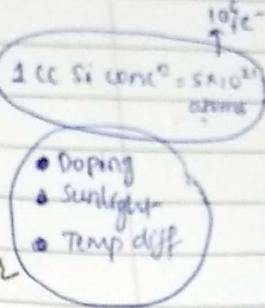
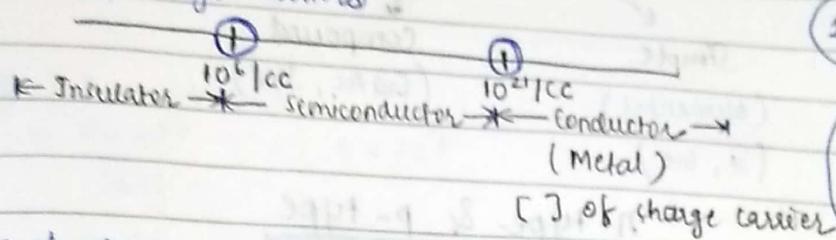
- ① Polarity of charge carriers
- ② Concentration of charge carriers




③ Transport of charge carriers.

- So, the conclusion is — in metal, current is only due to potential gradient, i.e. only drift current present
- In semiconductor, all 3 types of current - ① drift ② diffusion & ③ Thermoelectric currents are present, so semiconductor can be used design different kinds of materials.

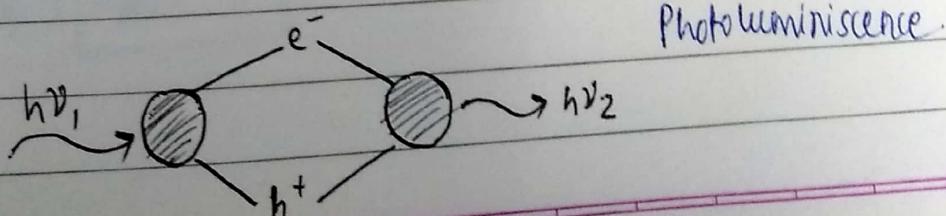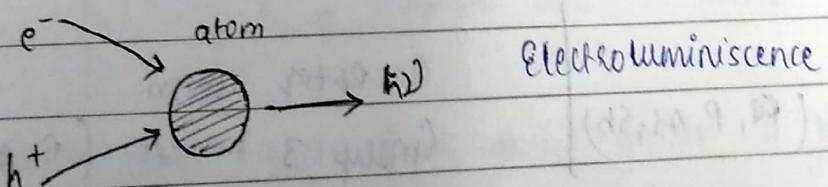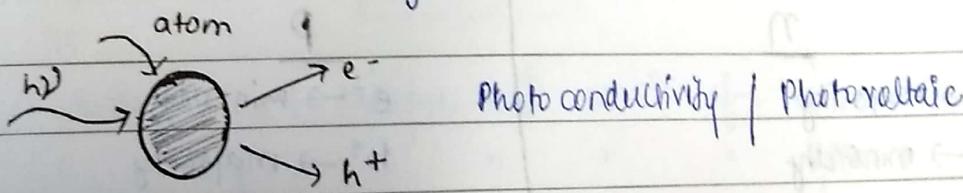④ Interaction with electromagnetic field.



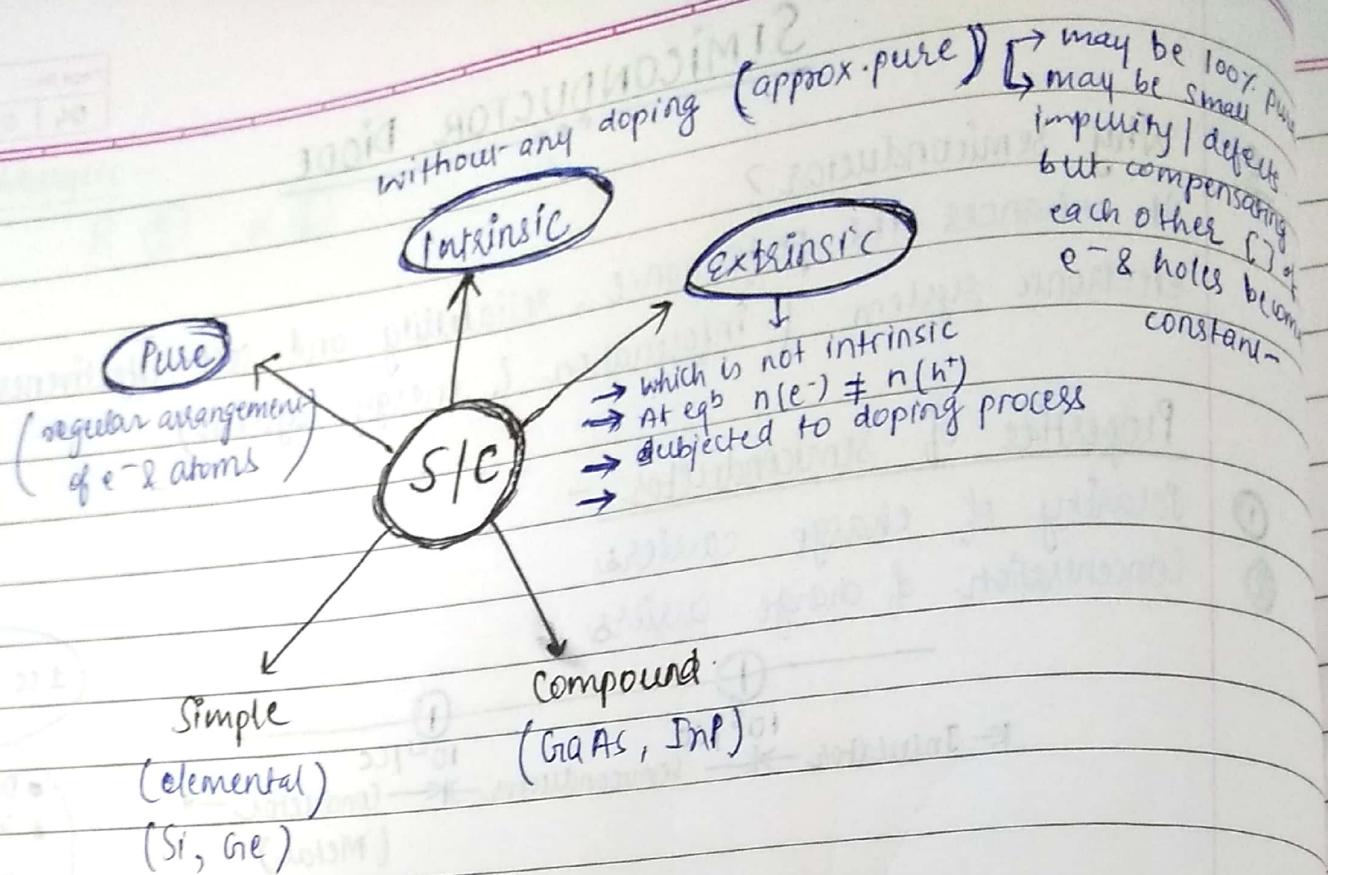

n-type & p-type

n-type - (Donor) -

Any n-type can be created by introducing impurity element that has 5 valency e^- such as Sb, As, P.

p-type - (Acceptor) -

Any p-type is formed by doping a pure Ge/Si crystal with impurity atoms having 3 valence e^- s. The elements most frequently used are Be, Ga, Al, In.

n
 $e^- \rightarrow$ majority
 $h^+ \rightarrow$ minority

donor atom

Group 5 mixed (N₅, P, As, Sb)

p
 $e^- \rightarrow$ minority
 $h^+ \rightarrow$ majority

acceptor atom

Group 3 mixed (B, Al, Ga, In)

→ [eq^b conc]

$$\text{Intrinsic } [] , n_i = 1.5 \times 10^{10} / \text{cc} = X (e^- / h^+)$$

$$\text{Atomic } [] = 5 \times 10^{22} / \text{cc} = Y.$$

$$\text{Ratio of } X \& Y = 1 e^- / h^+$$

for every 5×10^{11} Si atom

This is very low conc^b as compared to metal.

So, 'Si' is semiconductor

$$\text{Impurity } [] = 10^{15} / \text{cc}$$

$$\text{Ratio} = \frac{5 \times 10^{22}}{10^{15}} = 5 \times 10^7$$

i.e 1 impurity is present inside 5×10^7 atoms.

① Condition for impurity addition —

① Structure shouldn't change

② Impurity should be unaffected to each other (no force of interaction)

06/09/18.

The doping concentration ~~will~~ allow us to control the conc^b of free e⁻ & holes.

$$\text{At thermal eq^b, } [n_0 p_0 = n_i^2] \text{ law of Mass Action.}$$

where n_0 = thermal eq^b conc^b of free e⁻(s)

p_0 = " " " " holes

n_i = intrinsic conc^b = fixed.

At room temp, each donor atom donate a free e⁻ to the semiconductor

if $n_d \gg n_i$

$$n_0 \approx n_d$$


$$P_0 = \frac{n_i^2}{n_d}$$

Similarly, $P_0 \approx n_a$

$$\boxed{P_0 = \frac{n_i^2}{n_a}}$$

Law of mass action.

Semiconductor Diode

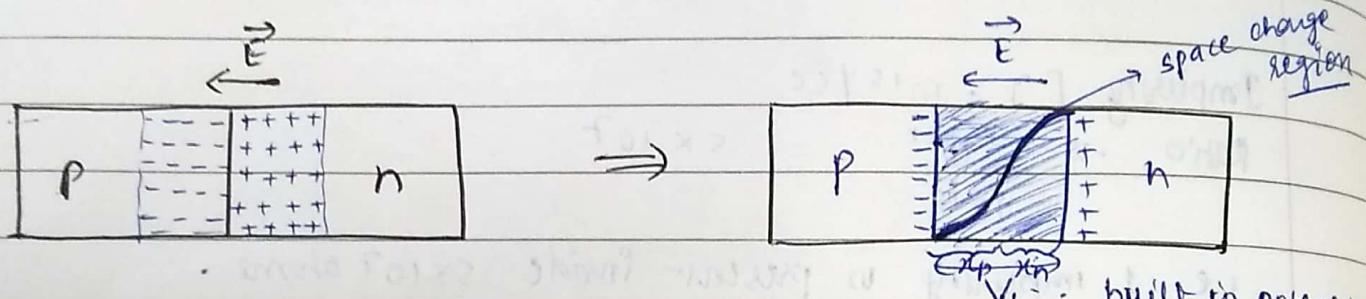

$\boxed{V_{bi} = \frac{kT}{q} \exp\left(\frac{N_a N_d}{N_i^2}\right) \approx 0.1 \text{ V}}$

↳ electronic charge

↳ ideal condition [0.2 V]

$$N_a = \text{acceptor conc}^2 = P_0$$

$$N_d = \text{donor conc}^2 = n_0$$

$$N_i = \text{intrinsic conc}^2$$


V_{bi} can't be measured by voltmeter (small V_{bi})

Charge neutrality - $A q N_a X_p = A q N_d X_n$ not symmetric


$$\boxed{\frac{X_p}{X_n} = \frac{N_d}{N_a}}$$

$= 10^{16} / 10^{15}$ [depends on donor conc²].

$$= 10^1$$

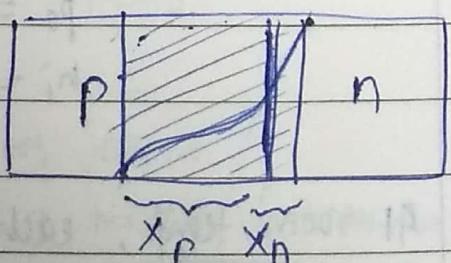

Reverse Bias

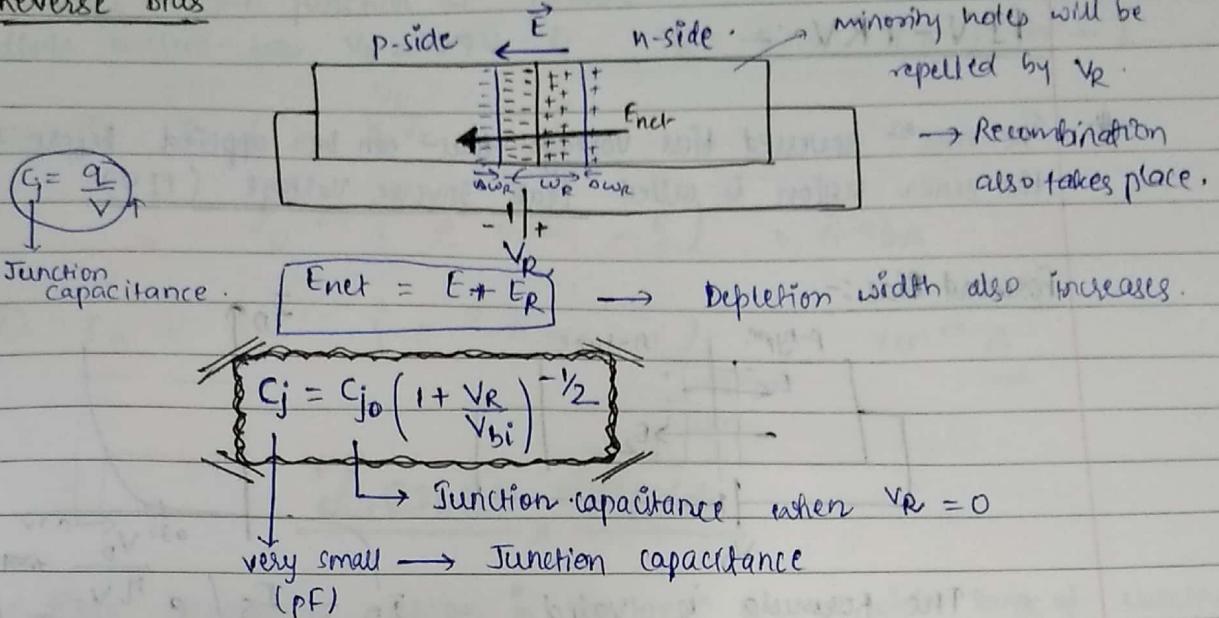

When a reverse biased voltage is applied to a p-n junction the \vec{E} in the space charge region increases due to this, very large \vec{E} , minority carriers get kinetic energy and thus, it collides with the covalent bond or crystal, it breaks the bond and e-hole pair is generated

e⁻ are swept into the n-region & holes are swept into p-region by the high electric field, generating a large reverse saturation current - (I_S). This phenomenon is called Breakdown.

① Avalanche Breakdown

- SIC is moderately (less) doped.
- Depletion layer is thick.
- \vec{E} is large, so e⁻ & holes will get K.E / acc². $a = \frac{eE}{m}$

- Applied V_Z is around 12-14V which is large as compared to Zener.


② Zener Breakdown

- SIC is heavily doped.
- Depletion layer is very thin.
- \vec{E} is very large.
- Applied V_Z is around 6V which is less as compared to avalanche.


PIV - PRV :-

The max^{is} reversed bias voltage that can be applied before entering the zener region is called Peak Reverse Voltage (PIV)

Forward Bias :-

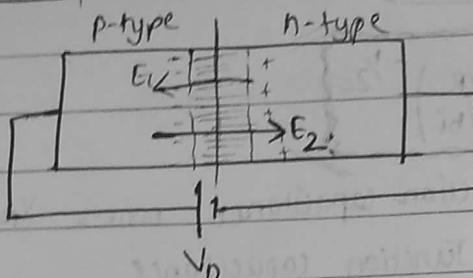

$I_D \uparrow$

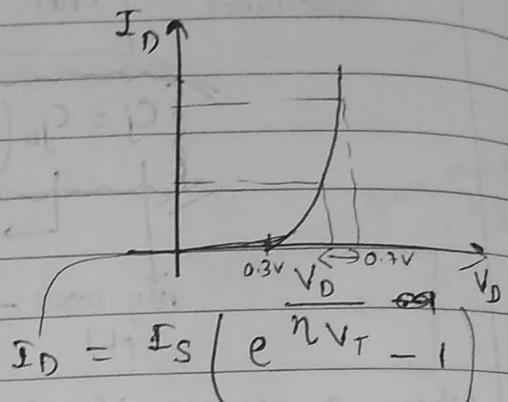

The formula is valid
only if $E_{\text{net}} = E_1 - E_2 \geq 0$

I_D = diode current-

I_S = saturation current-

V_D = diode voltage

$V_T = \frac{kT}{q} = 0.026 \text{ volt}$

η = ideality factor, for Si=1
 η =2

Q Calculate the junction capacitance of p-n junction.

Consider a Si p-n junction at $T = 300K$, with doping concn

$N_A = 10^{16}/\text{cc}$ & $N_D = 10^{15}/\text{cc}$. Assume that $n_i = 1.5 \times 10^{10}/\text{cc}$

& $C_{j0} = 0.5 \text{ pF}$. Calculate C_j at $V_R = 1V$ & $V_R = 5V$.

Sol? - $V_{bi} = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right) = 0.637$ $V_T = \frac{kT}{q}$

① $C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$ $V_R = 1$
 $= 0.312 \text{ pF}$ $C_j \downarrow V_R \uparrow$

② $C_j = 0.168 \text{ pF}$ $V_R = 5$

$$V_D = 0.7V$$

Q Consider a p-n junction at $T=300K$ in which $I_S = 10^{-14}$, find the diode current for $V_D = 0.7V$ & $V_D = -0.7V$ [$\eta = 1$ for Si]


$$\textcircled{1} I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$= 10^{-14} \left(e^{\frac{0.7}{0.026}} - 1 \right) = 4.93A$$

$$\textcircled{2} I_D = 10^{-14} \left(e^{-\frac{0.7}{0.026}} - 1 \right) = 10^{-14} A$$

Zener Diode

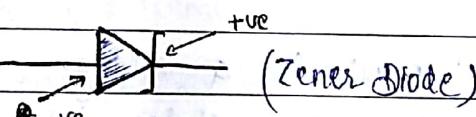The diode breakdown voltage is constant over a wide range of current.




V_Z = Zener breakdown voltage

I_Z = Reversed bias current when diode is in breakdown region.

I_{Zm} = Max current that zener diode can sustain.

a) V_i , R , & R_L all fixed

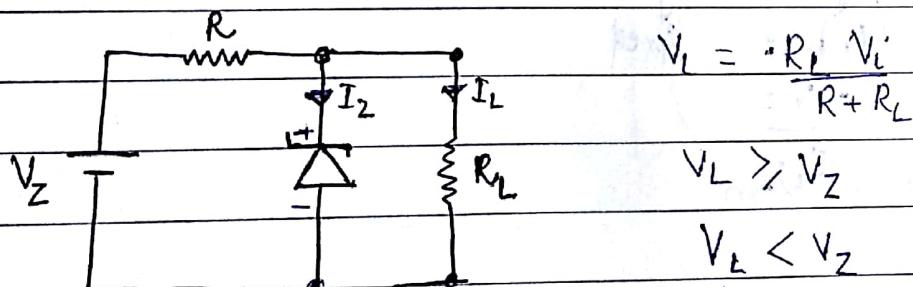


$$V_Z = V_L$$

$$I_Z = I_R - I_L$$

$$= \frac{V_i - V_Z}{R} - \frac{V_Z}{R_L}$$

② V_i fixed & R_L is variable. -

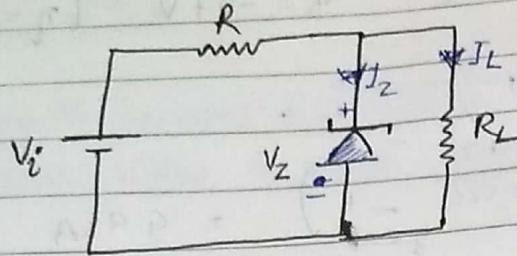

$$V_Z = V_L = \frac{V_i R_L}{R + R_L}$$

$$R_L = \frac{R V_Z}{V_i - V_Z}$$

for which zener diode is
in active mode.

$$(I_L)_{\max} = \frac{V_L}{(R_L)_{\min}}$$

$$(I_L)_{\min} = I_R - I_{ZM}$$

If $V_L \geq V_Z \rightarrow \text{ON}$
 $V_L < V_Z \rightarrow \text{OFF}$

$$\begin{cases} I_{ZM} \\ P_{ZM} \end{cases}$$

always remember
in case of
zener.

Two small R_L will result in a voltage V_L across the load resistance $< V_Z$ and the zener diode will be in 'OFF' state

Any load resistance $> R_L$ will ensure that zener diode is in ON state and it can be replaced by V_Z .

$$(I_L)_{\min} = I_R - I_{ZM}$$

$$\begin{matrix} \downarrow \\ (R_L)_{\max} \end{matrix} \quad \begin{matrix} \downarrow \\ \text{fixed} \end{matrix}$$

$$= \frac{V_Z}{(I_L)_{\min}}$$

③ R_L is fixed and V_i is variable. -

$$\checkmark V_L = V_Z = \frac{R_L V_i}{R + R_L}$$

$$(V_i)_{\min} = \frac{(R + R_L) V_Z}{R_L}$$

$$\checkmark (V_i)_{\max} = I_R R + V_Z = (I_{Z\max} + I_L) R + V_Z$$

DC gives average nature of signal.


Page No.:

Ex(1) For given zener diode network, determine V_L , V_R , I_Z , P_Z .

Sol:- $V_L = 16 \times \frac{V_Z}{R_{Z1} + R_{Z2}} = 8.72 \text{ V}$

$$V_R = I \times R = 1 \times \frac{160}{2 \times 11} = 7.27 \text{ V}$$
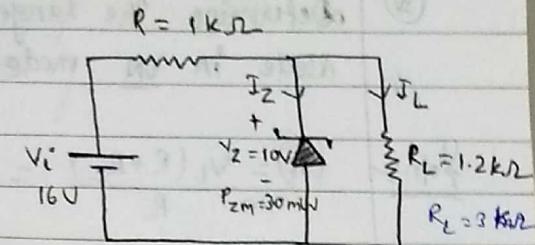
$$I_Z = \frac{P_{Zm}}{V_Z} = \frac{30}{10} = 3 \text{ mA}$$



$$V_L = 10 \text{ V}$$

$$V_R = 6 \text{ V}$$

$$I_Z = 2.67 \text{ mA}$$

$$P_Z = V_Z I_Z = 10 \times 2.67 = 26.7 < P_{Zm}$$

(only to compare)


Ex(2) For a given network, a) determine the range of R_L & I_L that will result in V_R being maintained at 10V.

b) determine the max^m wattage rating of diode.

a) $V_L = \left(\frac{R_L}{R_L + R} \right) V_i = 10$

$$R_L \times 50 = 10R_L + 10 \times 1$$

$$(R_L)_{\min} = 0.25 \text{ k}\Omega$$

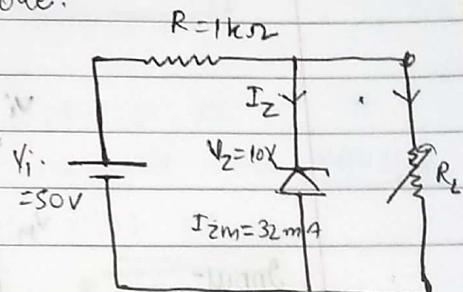

$$(R_L)_{\max} = \frac{V_Z}{I_{L\min}}$$


$$= \frac{10}{8}$$

$$= 1.25 \text{ k}\Omega$$

$$\begin{aligned} (I_L)_{\min} &= I_R - I_{Zm} \\ I_R &= \frac{V_R}{R} = 40 \text{ mA} \end{aligned}$$

$$40 - 32 = 8 \text{ mA}$$

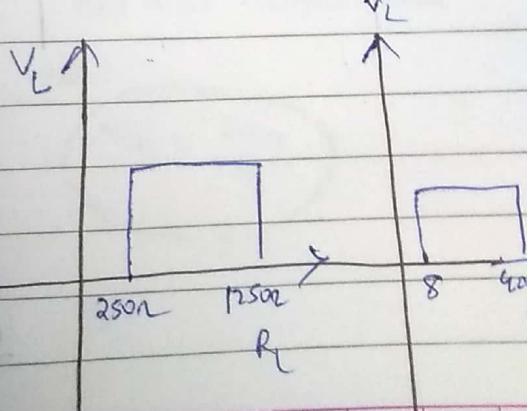b) $P_{\max} = V_Z I_{Zm}$
 $= 10 \times 32$
 $= 320 \text{ mW}$



$$FT \ L T \ Z T \ W T \ D C \ T \ W T \ H T$$

Time & Spatial domain

$$X(w) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt \rightarrow \text{Fourier transform}$$

$$\omega = 0 \Rightarrow DC \quad X(0) = \sum_{n=0}^{\infty} x[n]$$

Page No.:

(B) Determine the range of value of V_i that will maintain zener diode in 'ON' mode.

Soln:-



$$(V_i)_{\min} = \frac{V_L(R + R_z)}{R} = 23.67 V$$

$$(V_i)_{\max} = I_R R + V_Z = (I_{Zm} + I_L) R + V_Z$$



$$= (60 + 16.67) \times 220 + 20$$

$$= 36.87 V$$
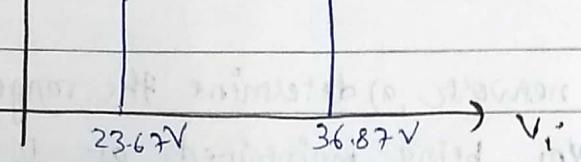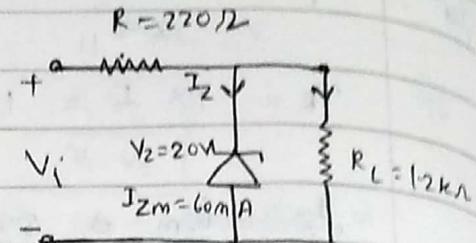
$$I_L = \frac{V_L}{R_L} = \frac{200}{12} = 16.67 \text{ mA}$$



RECTIFIER

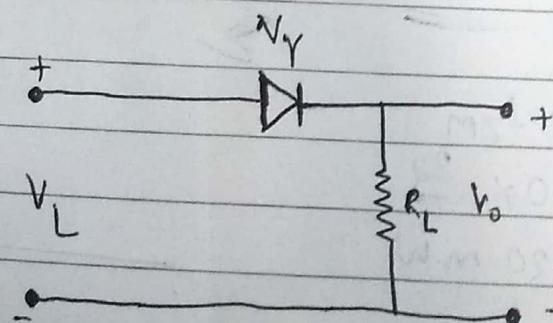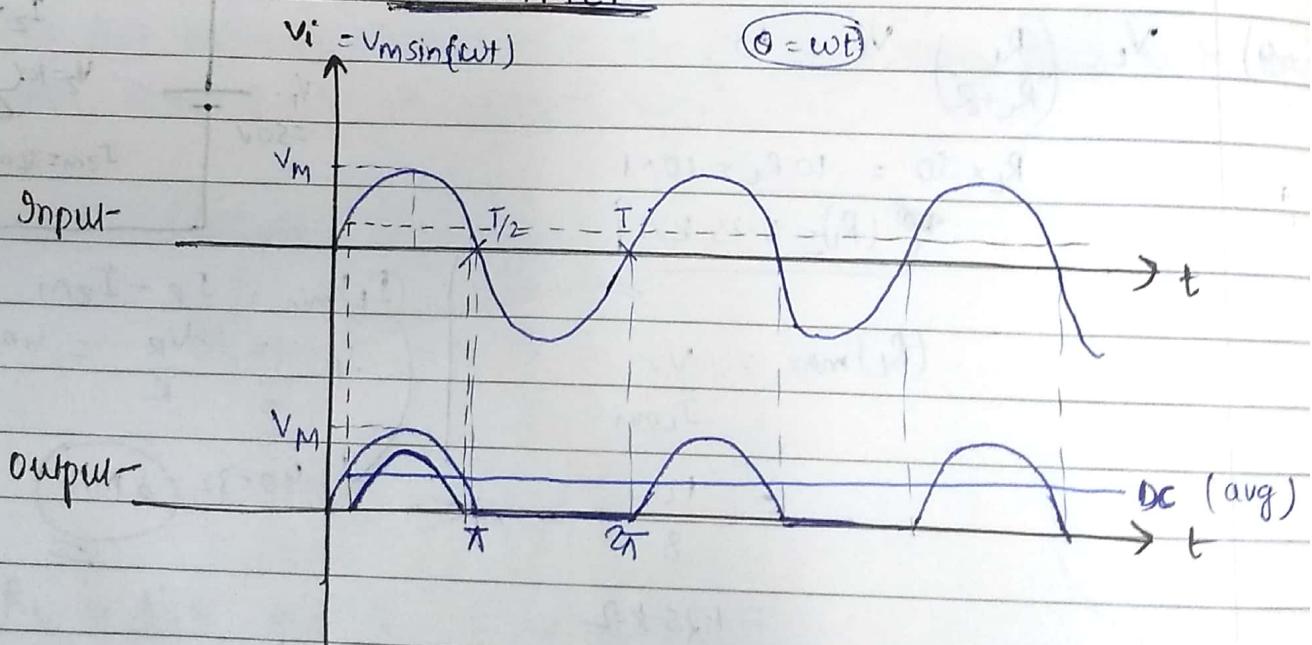


$$V_{avg} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta$$

$$= \frac{V_m}{2\pi} \left(\int_0^{2\pi} \sin \theta d\theta + \int_0^{2\pi} \theta d\theta \right)$$



$$\boxed{V_{avg} = V_{dc} = \frac{V_m}{\pi}} = 0.318 V_m$$

↓ pulsating dc ~~at~~ avg value = const.

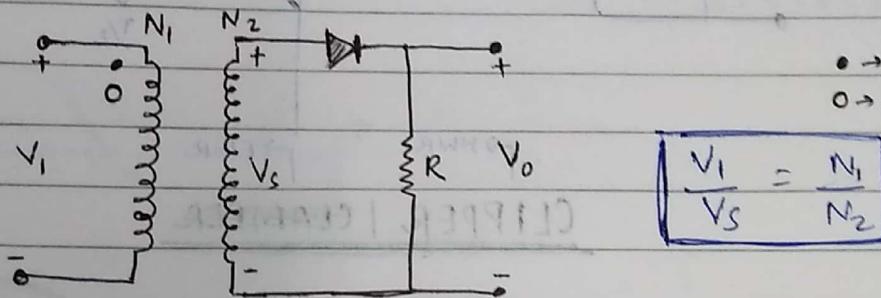
(Def) # Rectifier converts bipolar signal into unipolar signal or converts AC into pulsating DC.



FULL WAVE RECTIFIER

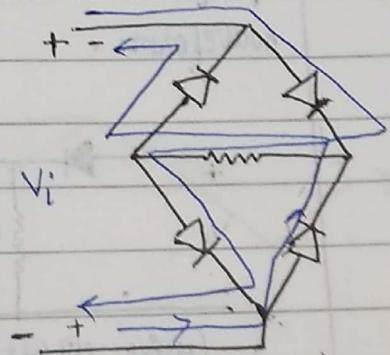
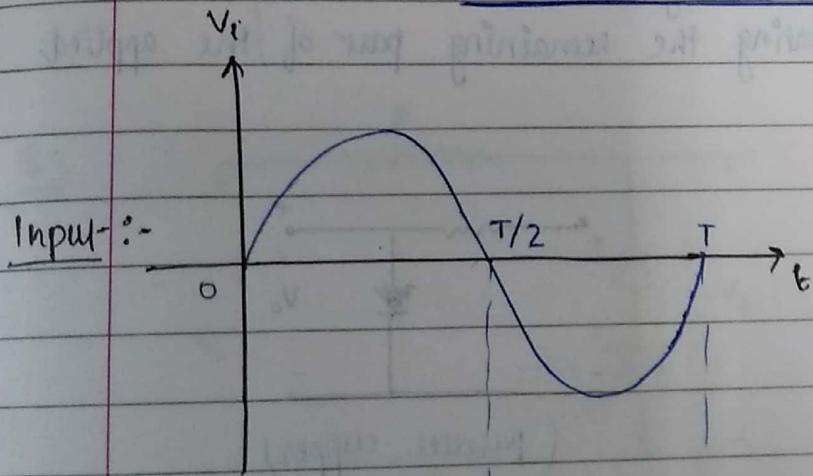


full wave rectifier circuit

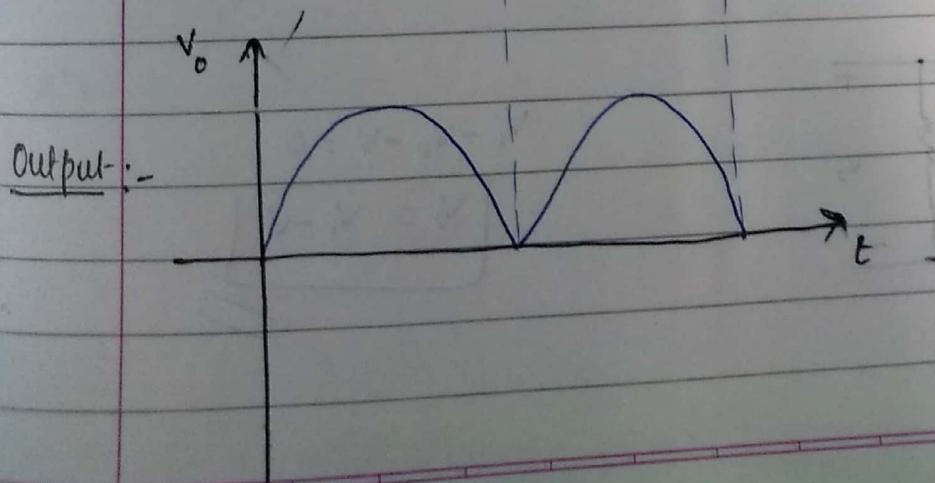


$$V_{dc} = \frac{2V_m}{\pi}$$

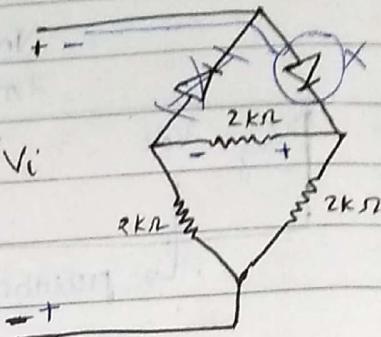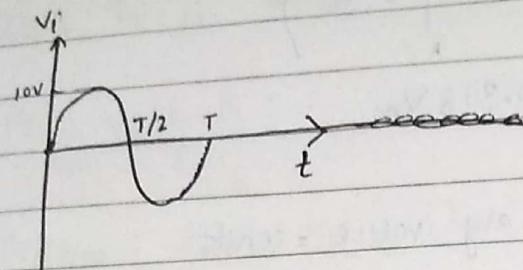
Q. Determine the output waveform for the given network, calculate the output dc level



For (+ve) half cycle -



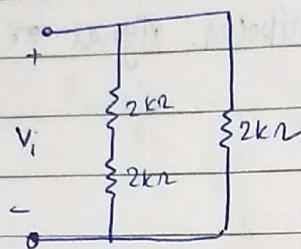

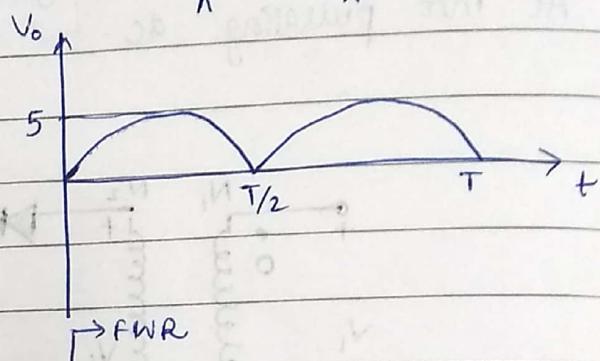
$$V_{dc} = \frac{2 \times 5}{\pi} = \frac{10}{\pi} = 3.18V$$





CLIPPER | CLAMPER

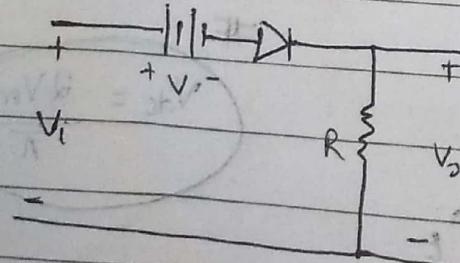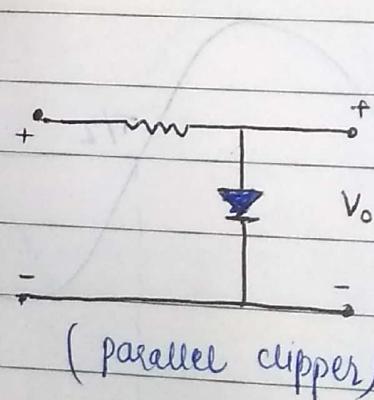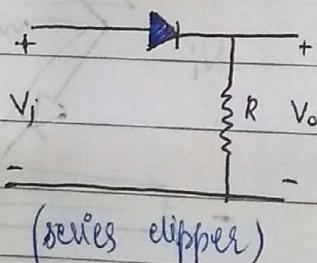In case of clipper circuit, half wave rectifier is a clipper circuit which eliminate portions of a signal that are above or below a specified level without distorting the remaining part of the applied waveform.



$$V_i - V_o - V = 0$$






$$V_o = V_i - V$$

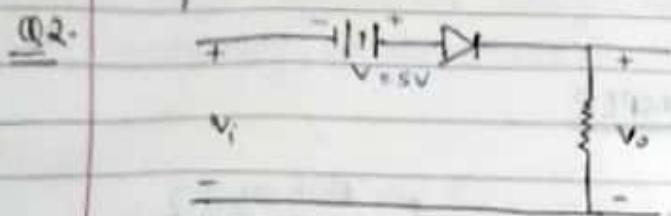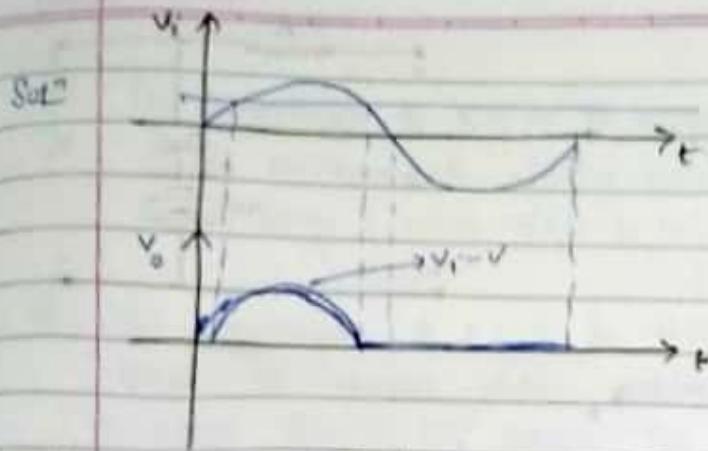


$$V_i + V = V_o$$

$$V_o = 20 + 5 = 25 \text{ V}$$


$$V_o = 0 + 5 = 5 \text{ V}$$

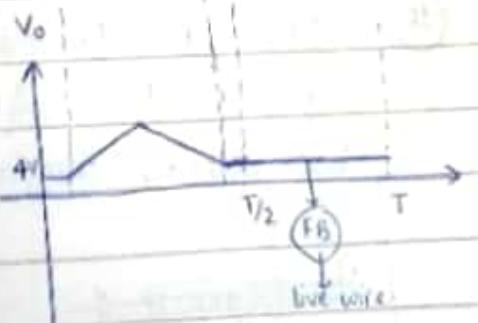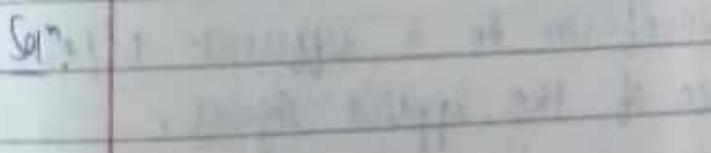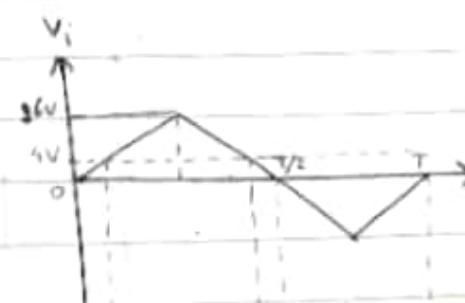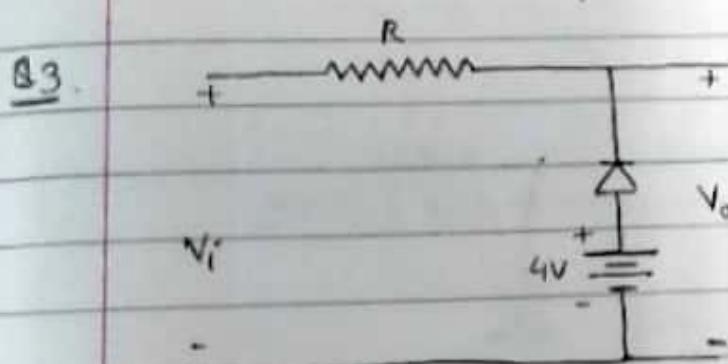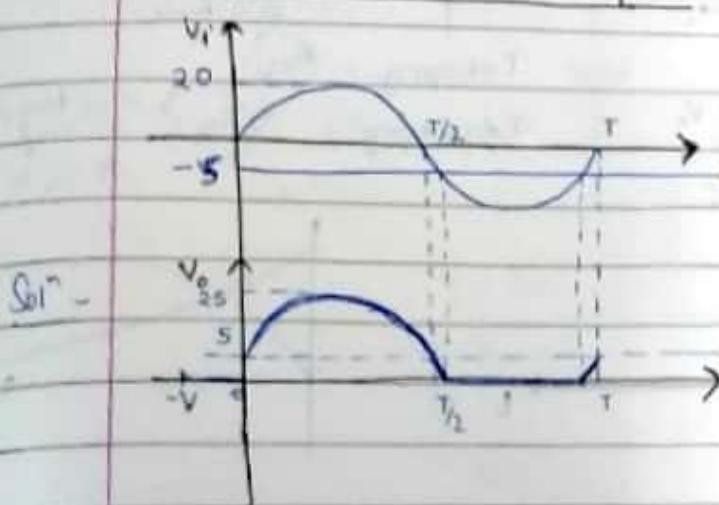

Q4

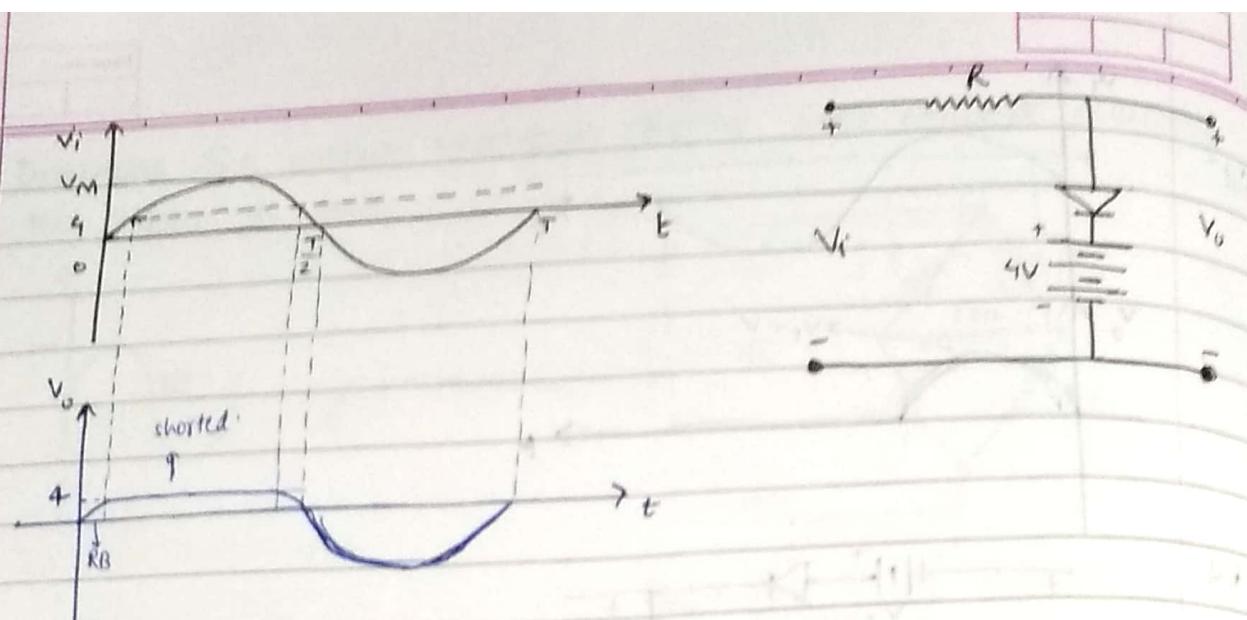


CLAMPER

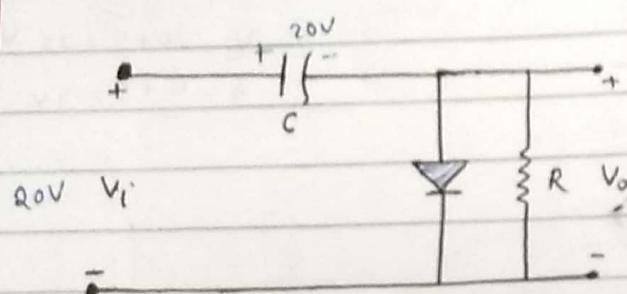

$$\tau_{\text{charging}} = R_{\text{eq}} C \quad \rightarrow \text{fast charging very small}$$
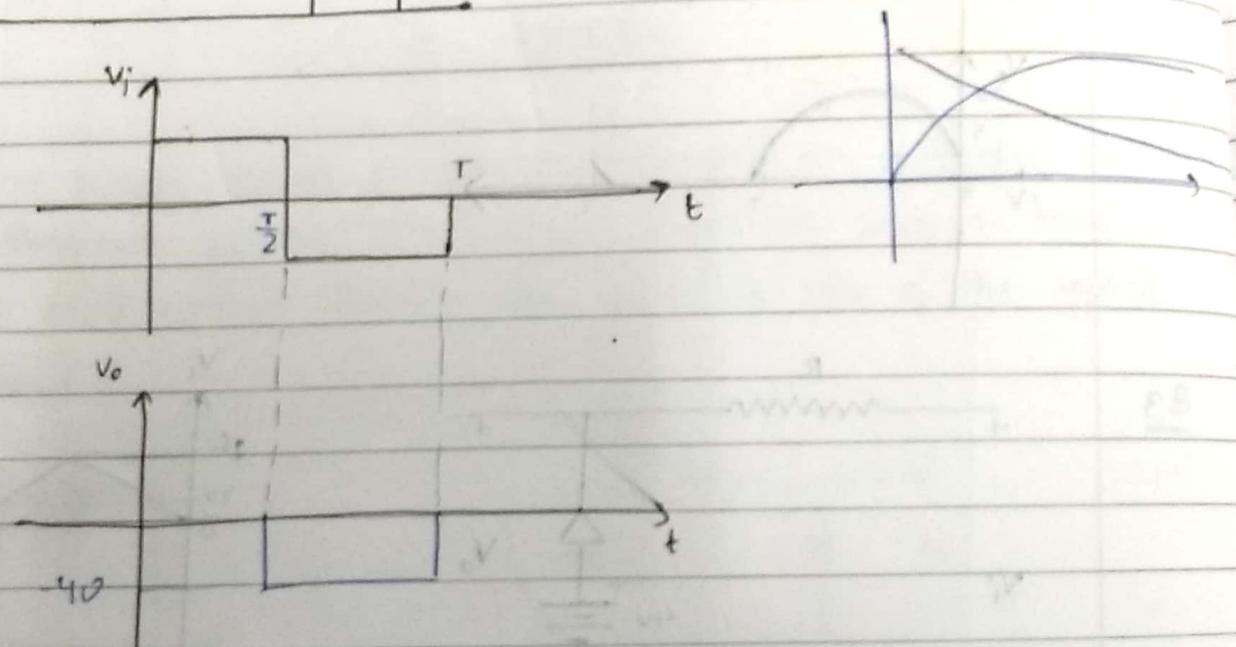
$$\tau_{\text{discharging}} = R_{\text{eq}} C \quad \text{Very long, as compared to } T/2 \text{ to } T$$





Clamper is a network constructed of a diode, a resistor and a capacitor that shifts/clamps a waveform to a different DC/AC level without changing the appearance of the applied signal.

our aim is to get max output

Page No.:

The magnitude of R & C is chosen such that $T = RC$ is sufficiently small so that to ensure that capacitor become charged immediately. (when diode is in forward biased)

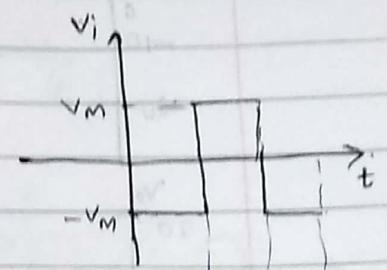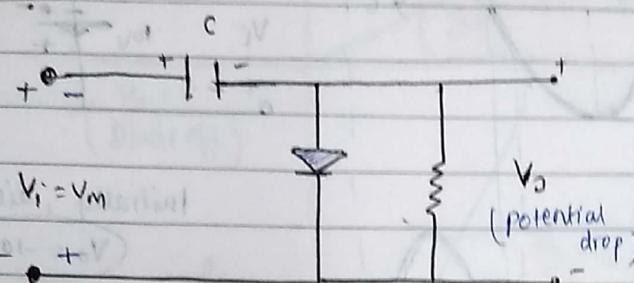The magnitude of R & C is chosen such that $T = RC$ is sufficiently large to ensure that voltage across capacitor does not discharge significantly during the interval, the diode is not conducting. (when diode is in reverse biased)





$$V_i = V_c$$

(net swing is same)

$$-V_m - V_c - V_o = 0$$

$$V_o \approx -2V_m$$

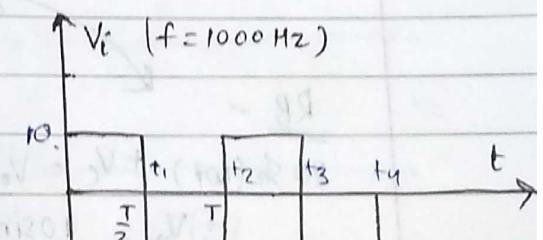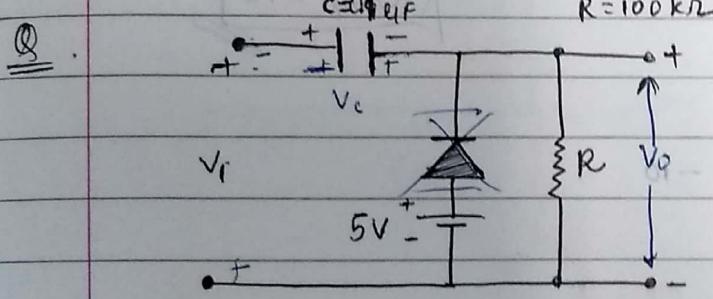

diode \rightarrow forward $-20\text{V cycle } (t_1 \rightarrow t_2)$

$$-V_i + V_c - 5 = 0$$

$$V_c = V_i + 5 = -25$$

signs is already considered

diode \rightarrow reverse $+10\text{V cycle } (t_2 \rightarrow t_3)$



$$V_i + V_c = V_o$$

$$10 + 25 = 35 = V_o$$

Short circuit $\Rightarrow 0.7V$ (of diode) Page No.:

$$T_{charging} = RC = 100 \text{ k} \times 1 \mu\text{F} = 10 \text{ ms}$$
$$T_{discharging} = 5T_{charging} = 50 \text{ ms}$$
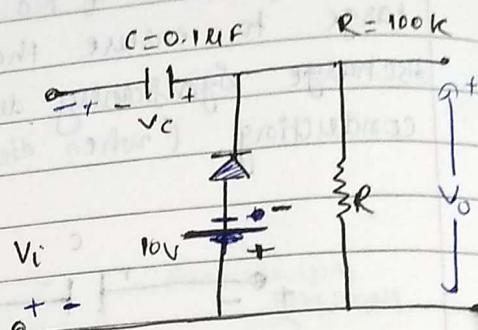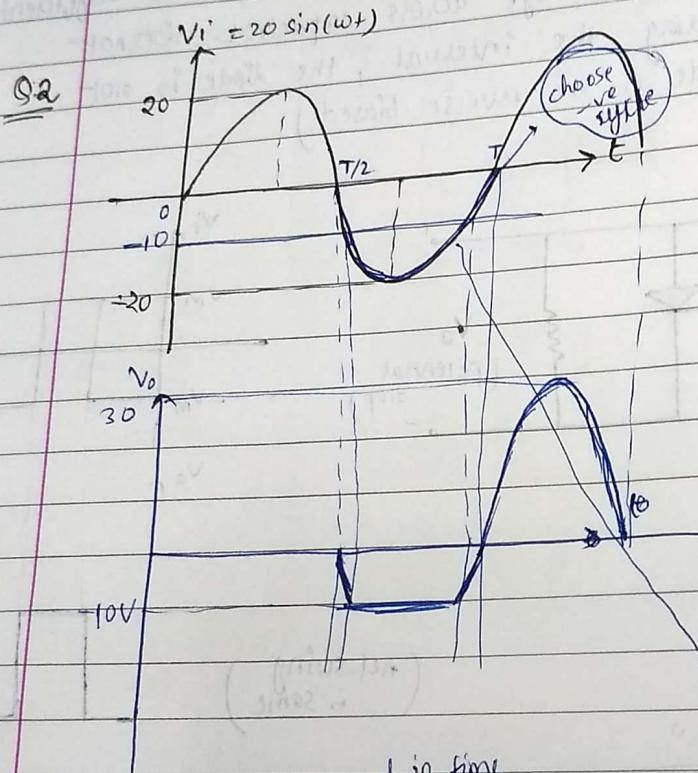
$$(t_2 \rightarrow t_3) = \frac{1}{2000} = 0.5 \text{ ms}$$



Initially, diode $\Rightarrow RB$

$$V_o = -10V$$

We have to select that part of ^{input} voltage for which diode is in forward biased

FB -

$$-20 \sin(\omega t) + V_c + 10 = 0$$

$$V_c = 20 \sin(\omega t) - 10$$

$$\boxed{(V_c)_{max} = 10}$$

RB -

$$20 \sin(\omega t) + V_c = V_o$$

$$V_o = 40 \sin(\omega t) - 10$$

$$(V_o)_{max} = 30$$

used in time of discharging

Storage potential difference of capacitor is used (while discharging)


← H T →

15 例 2

clippings


94

6

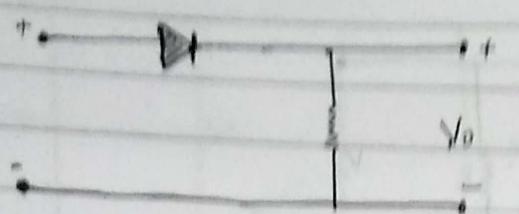

Find $\partial \mathcal{P} / \partial x$

(Smith Clapp)

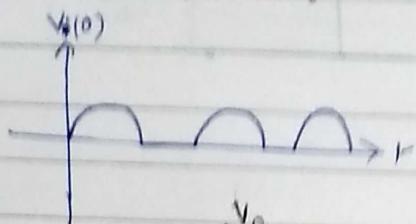


$v_0 = v_1$ (symm) \approx

$$V_0 = 0 \quad \text{RB}$$

Transfer characteristics


A graph showing the relationship between output voltage V_o (y-axis) and input voltage V_i (x-axis). The curve is piecewise linear, representing a diode's behavior. It is horizontal at a negative V_o value for $V_i < 0$, labeled '(Diode off)'. At $V_i = 0$, it jumps to a positive V_o value, labeled ' $V_o = V_0$ '. For $V_i > 0$, the curve is a straight line with a positive slope, labeled '(Diode ON)'.

Q

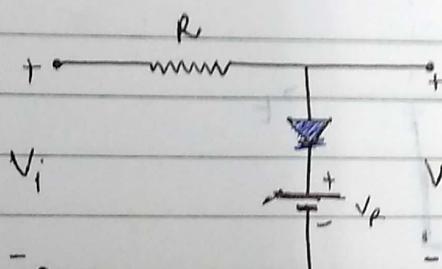


$m > n$


(11 dipper)

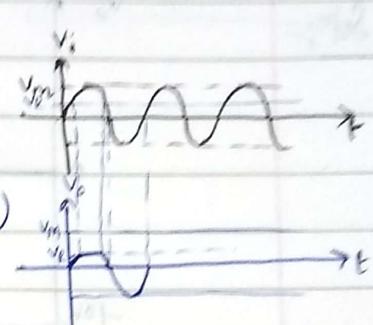

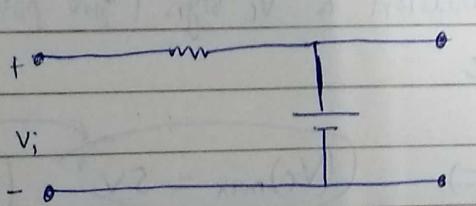In case of clipper problems, input signals should not be distorted.



(an)

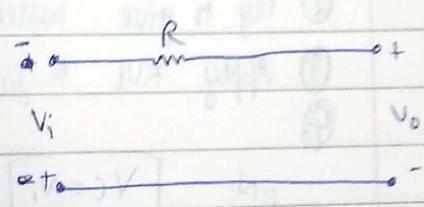

(PDF)

